

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE- SEMESTER-I & II(NEW)EXAMINATION – SUMMER 2022****Subject Code:3110016****Date:24-08-2022****Subject Name:Basic Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		Marks
<b>Q.1</b>	(a) What is a diode? Write its types and applications.	<b>03</b>
	(b) Explain the diode V-I characteristics of ideal and practical PN junction semiconductor diode.	<b>04</b>
	(c) Enumerate the different types of clipping circuits with their different names and input-output waveforms.	<b>07</b>
<b>Q.2</b>	(a) Why are junction transistors called bipolar devices?	<b>03</b>
	(b) The metal lead of the p-side of a p-n diode is soldered to the metal lead of the p-side of another p-n junction diode. Will the structure form an n-p-n transistor? If not, why?	<b>04</b>
	(c) Sketch the circuit of the common collector mode of BJT and its output characteristics. Derive the expression for the collector current and gain.	<b>07</b>
	<b>OR</b>	
	(c) Draw the fixed-biased circuit by considering an n-p-n transistor in the CE mode. Derive the expressions for stability factors. What are the functions of the coupling capacitors?	<b>07</b>
<b>Q.3</b>	(a) Write a short note on the optocoupler device?	<b>03</b>
	(b) Explain the sixteen segment display and its applications with the necessary circuit diagram.	<b>04</b>
	(c) Draw the approximate hybrid model for any transistor configuration at low frequencies. Show that only $h_{ie}$ and $h_{fe}$ are essential in the model. Is the approximation justified?	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) Explain the varactor diode.	<b>03</b>
	(b) Explain the construction of the solar cell with its operational principle.	<b>04</b>
	(c) What is self-bias? Draw the circuit showing self-bias of an n-p-n transistor in the CE mode. Explain physically how the self-bias improves stability.	<b>07</b>
<b>Q.4</b>	(a) What is MOSFET device? Draw its construction diagram.	<b>03</b>
	(b) Write short notes on the following : (i) Advantages of JFET (ii) Difference between MOSFET and JFET	<b>04</b>
	(c) Compare the different characteristics of the following semiconductor devices: bipolar junction transistor, field-effect transistor.	<b>07</b>
	<b>OR</b>	
<b>Q.4</b>	(a) How will you determine the drain characteristics of JFET? What do they indicate?	<b>03</b>
	(b) Explain the common drain configuration for a JFET.	<b>04</b>
	(c) Explain the JFET parameters and establish the relationship between them	<b>07</b>

- Q.5** (a) What is the thermal runaway in transistors, and how can it be avoided? **03**  
(b) What is an Early effect, and how can it account for the CB input characteristics?. **04**  
(c) What do you mean by the logic gate and its types? Explain the universal logic gates. **07**

**OR**

- Q.5** (a) What is the ac load line in the transistor? Write its significance. **03**  
(b) The value of alpha increases with the increasing reverse-bias voltage of the collector junction. Why? **04**  
(c) Explain the logic families and their types. Describe the characteristics of the same. **07**

\*\*\*\*\*